

# **HVDC Transmission Systems Based on Modular Multilevel Converters**

**Maryam Saeedifard**

**Georgia Institute of Technology**

([maryam@ece.gatech.edu](mailto:maryam@ece.gatech.edu))




PSERC Webinar  
February 3, 2015


# Presentation Outline

- **Introduction to HVDC Transmission Systems**
- **Converter Requirements for HVDC Transmission Systems**
- **The Modular Multilevel Converter (MMC)**
  - **Features**
  - **Operational Challenges**
  - **Solutions**
- **Future Work**
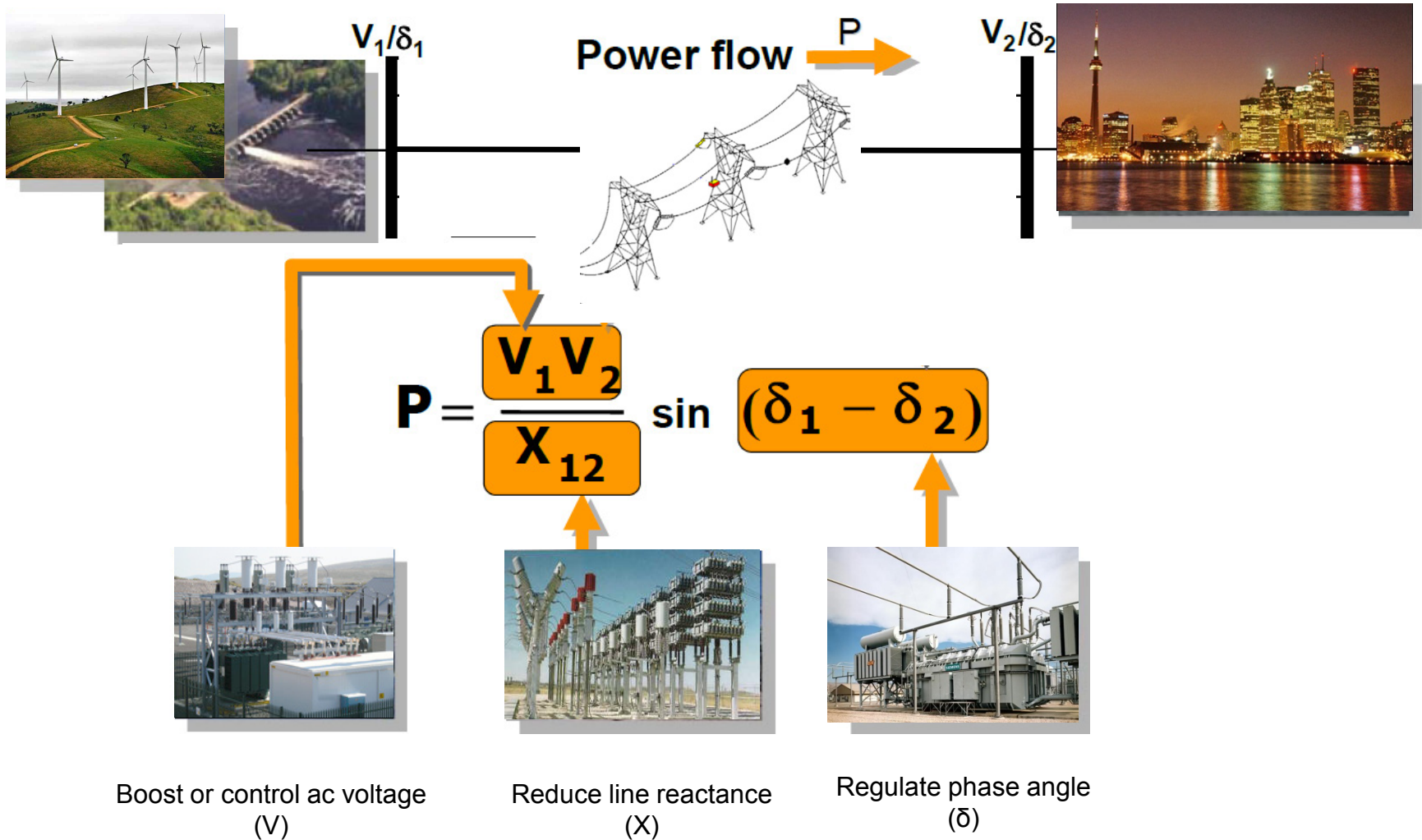
# Introduction: AC Corridor's Power Flow Control


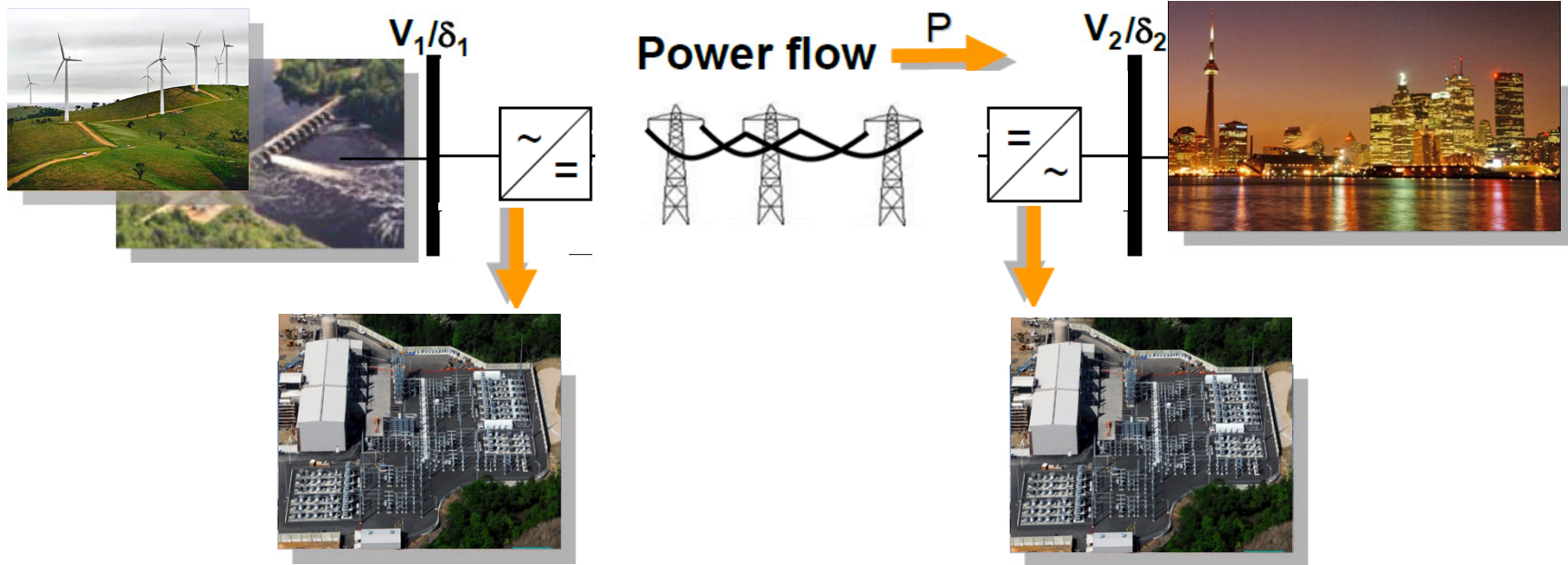
# Introduction: DC Corridor's Power Flow Control



$$P = V_{DC} \cdot I_{DC}$$

**HVDC**: High Voltage Direct Current Transmission

# Introduction: AC vs DC Transmission

## AC Transmission


- ✗ Loading a function of  $Z$
- ✗ Charging current a function of voltage level and cable capacitance
- ✗ Distance limitation
- ✗ 3 cables

## DC Transmission


- ✓ Power flow controlled
- ✓ No charging current effect or need for shunt compensation
- ✓ No distance limitation
- ✓ 2 cables
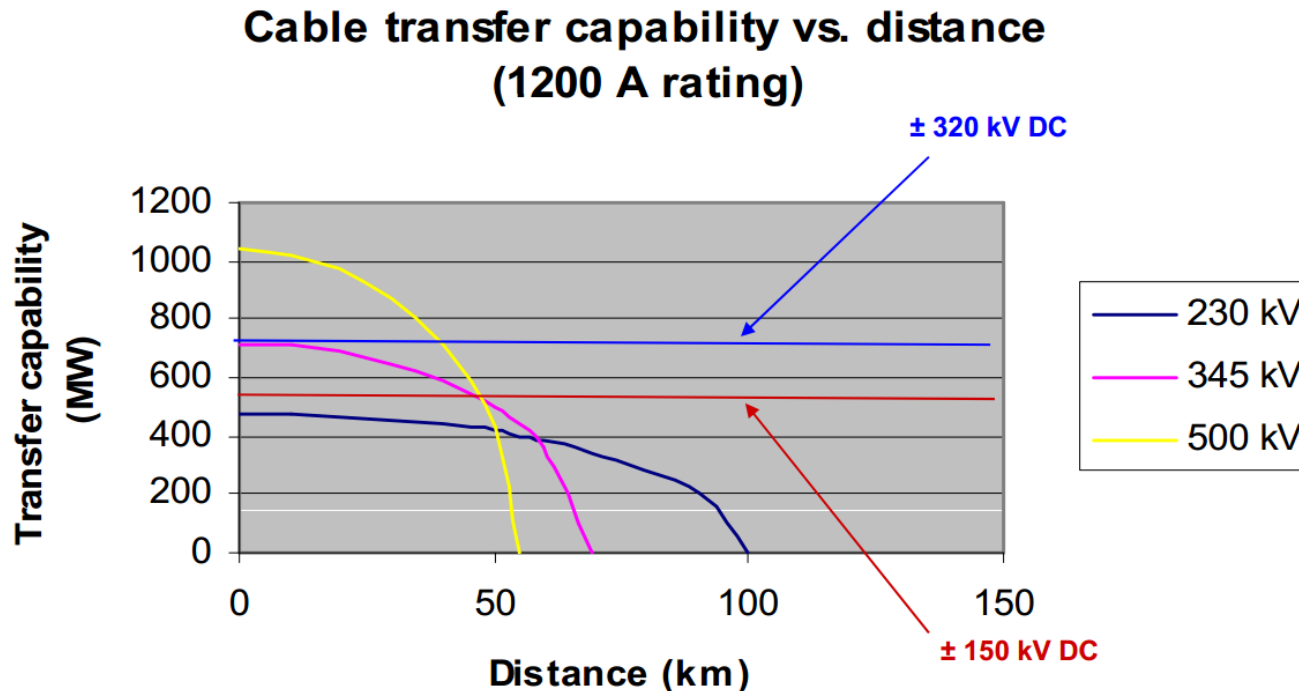
# Introduction: AC vs DC Transmission

- Due to reactive power charging, AC transfer capacity is dramatically reduced with distance
- DC transfer capacity is almost independent of distance



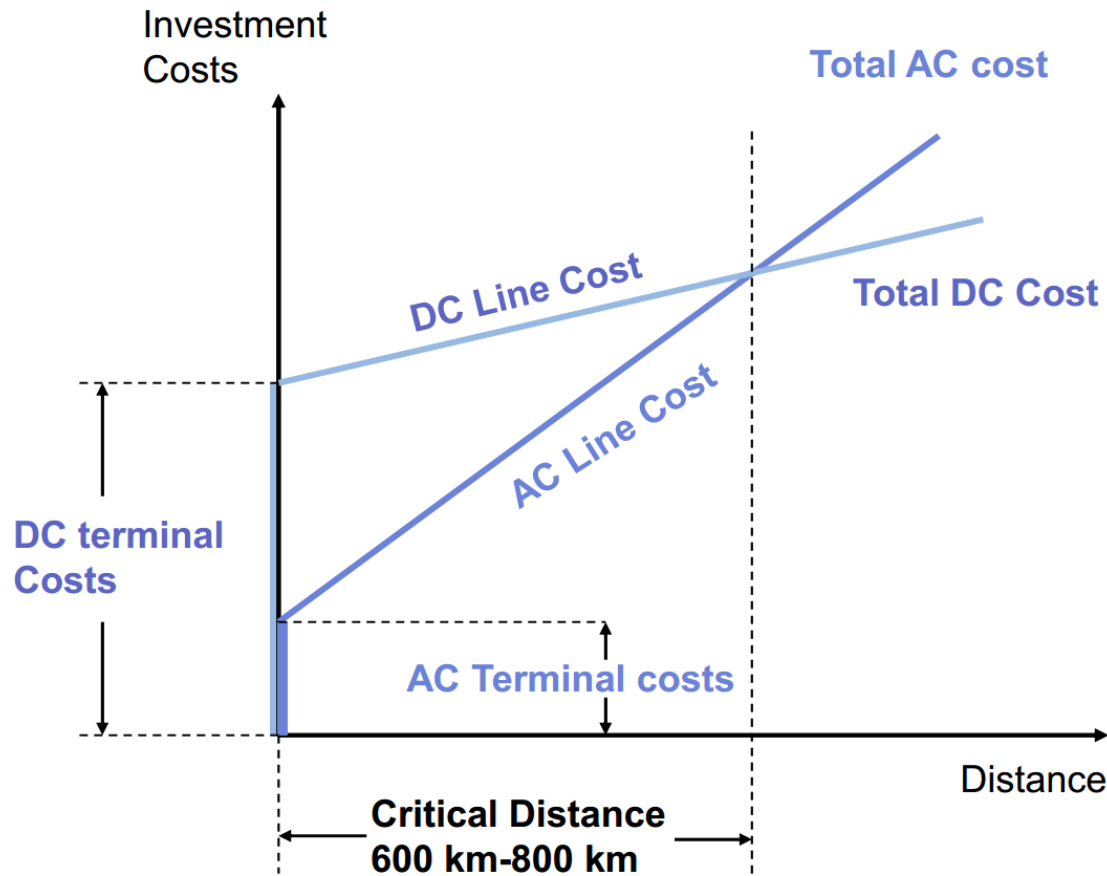
# Introduction: Overhead Line Transmission Investment vs Cost


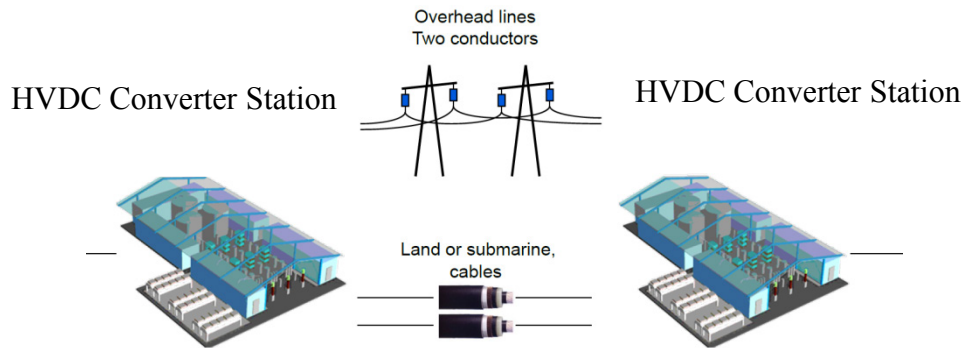
# Introduction: Types of HVDC Systems



- Point-to-Point Systems
  - Overhead lines
  - Subsea or underground cables




- Back-to-Back Systems
  - Interconnection of asynchronous AC grids



# Introduction: Basics of HVDC Systems

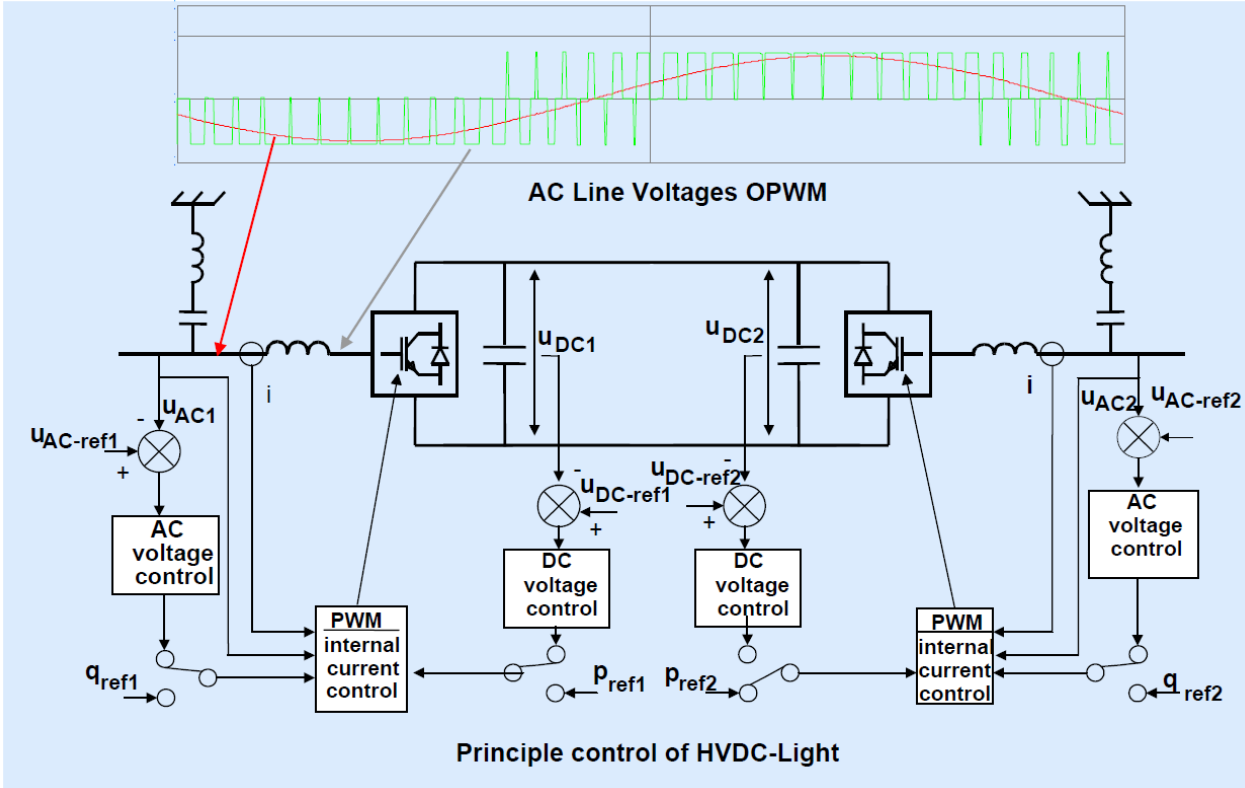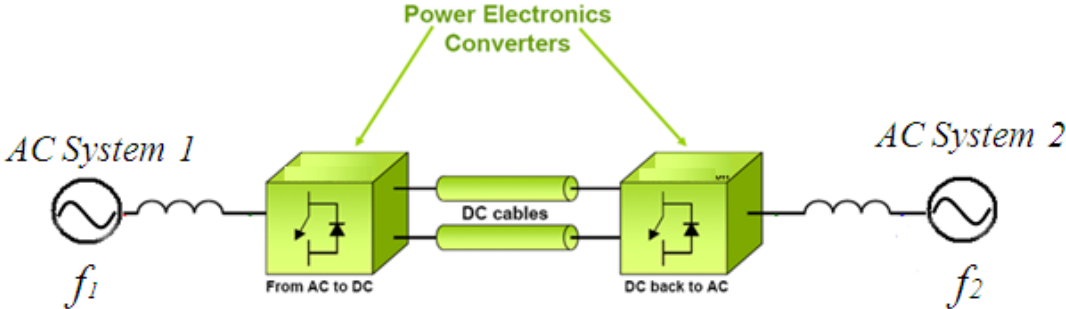

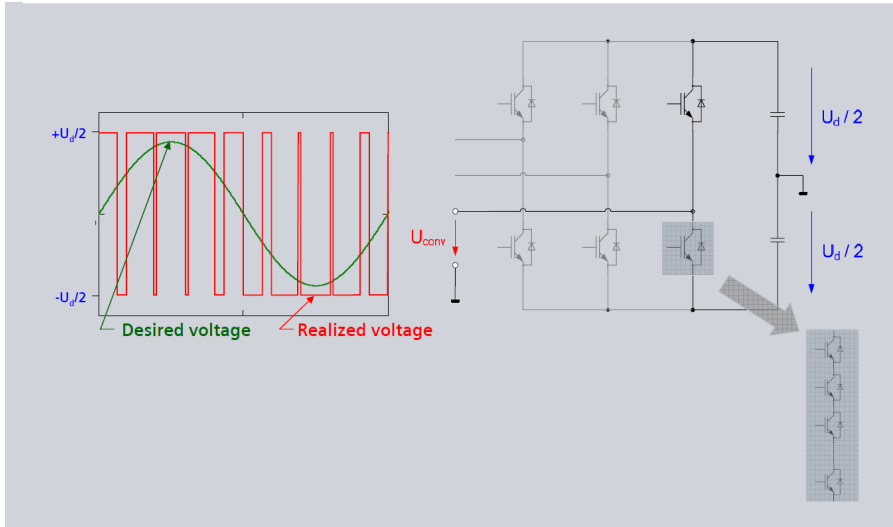
# HVDC Technology: Converter Requirements




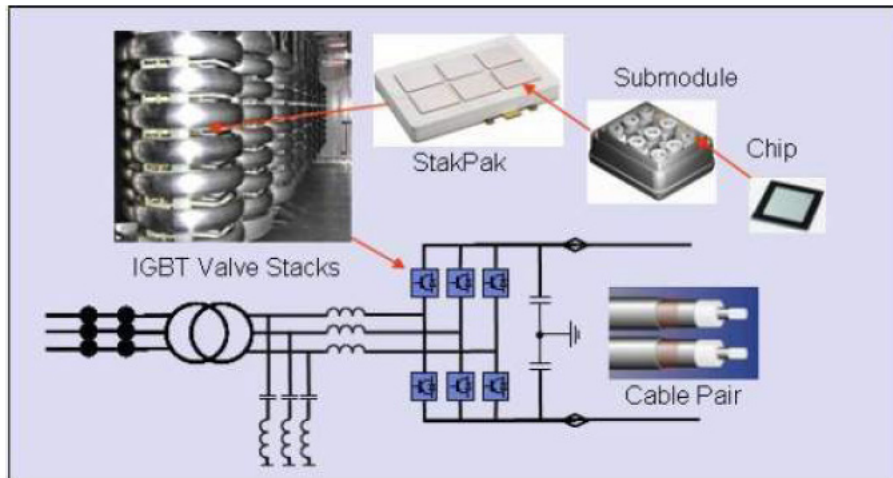
## Shortcomings:

- ✗ Harmonic distortion
- ✗ Switching frequency and power losses




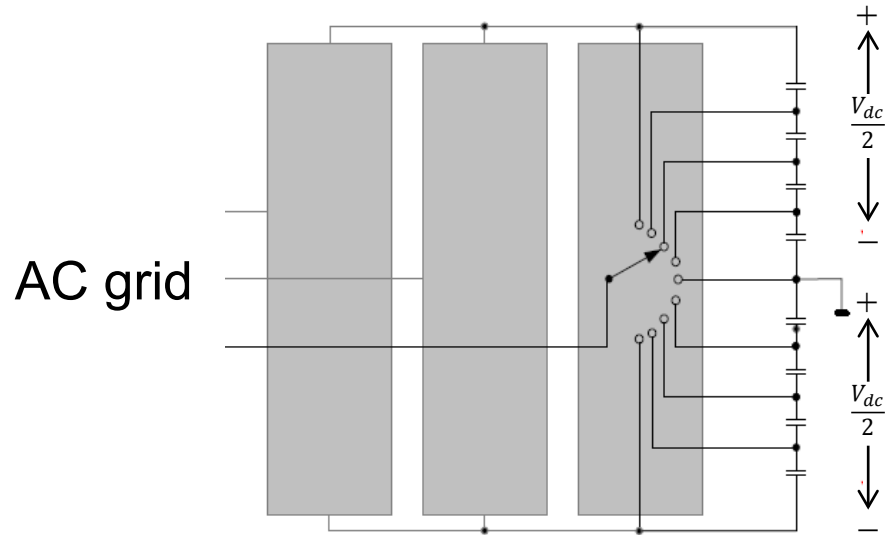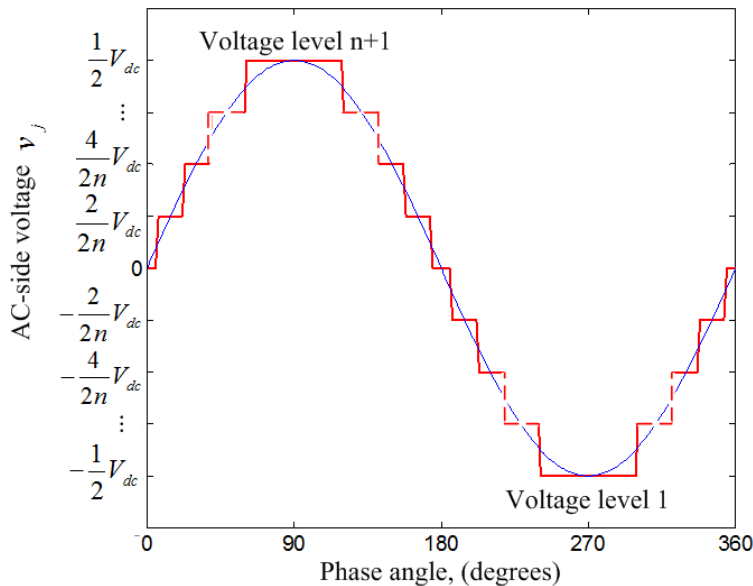
# HVDC Technology: Converter Requirements



- ✓ Staircase voltage waveform ==> Reduced harmonic distortion and filtering size
  - ✓ Low switching frequency ==> High efficiency

# The MMC

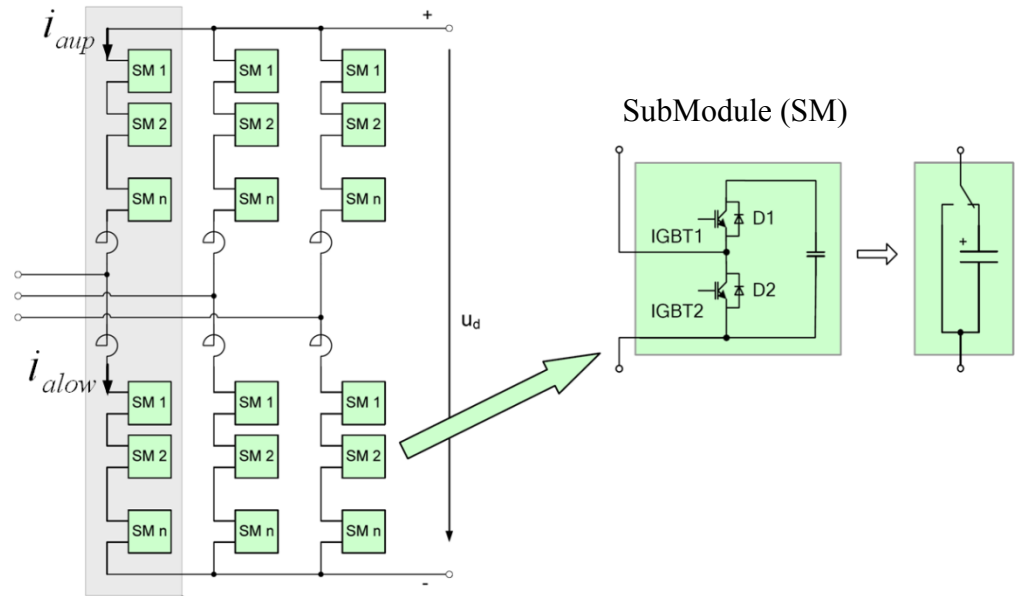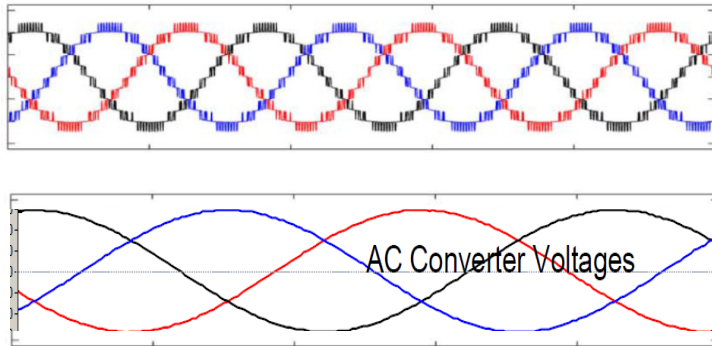



## Features:

- ✓ Modular and scalable design
- ✓ Smooth and sinusoidal waveform
- ✓ Increased reliability and redundancy

## Challenges:

- ✗ SM capacitor voltage balancing
- ✗ Circulating currents

# Equivalent Circuit of an MMC

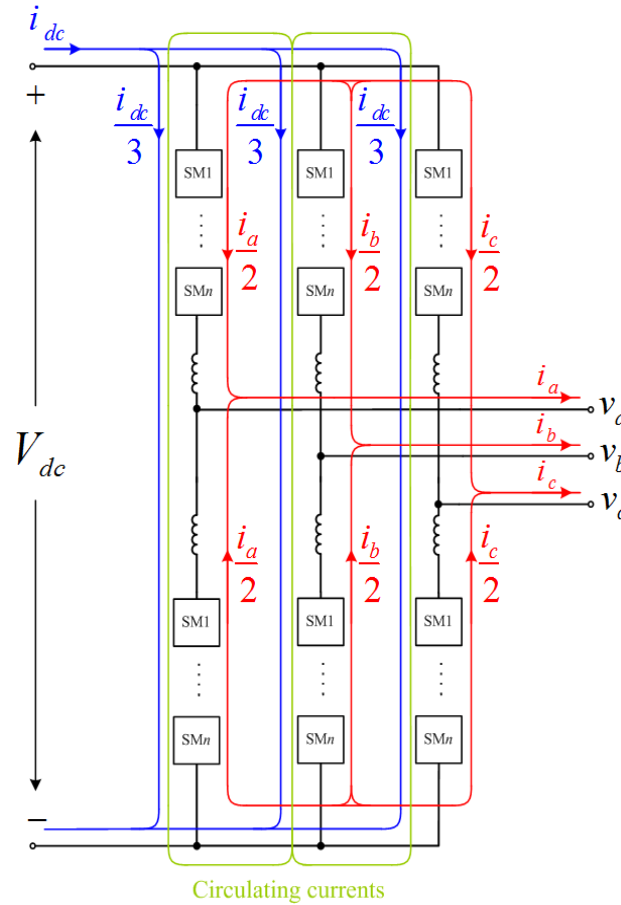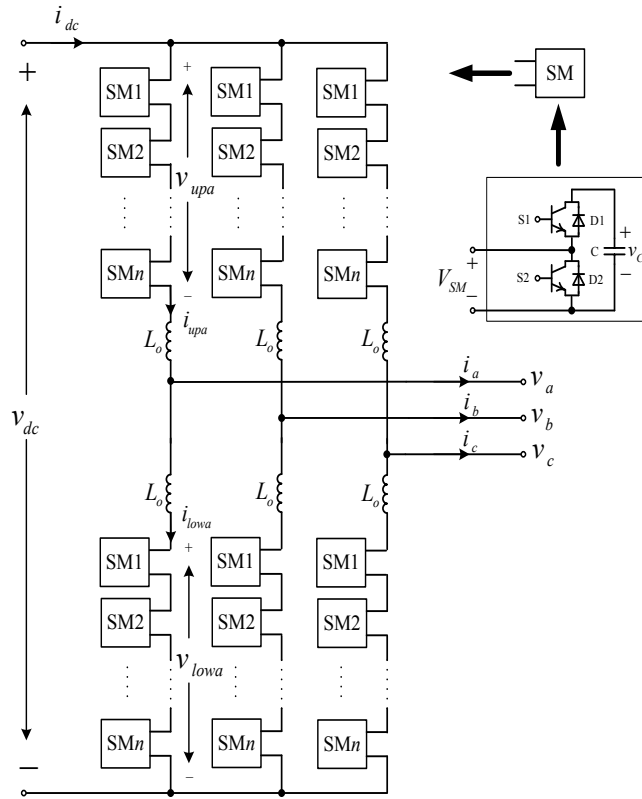

$$i_j = i_{upj} - i_{lowj}$$


$$i_{upj} = \frac{i_j}{2} + \frac{i_{dc}}{3} + i_{zj},$$

$$i_{lowj} = -\frac{i_j}{2} + \frac{i_{dc}}{3} + i_{zj},$$


$$i_{zj} = \frac{1}{2}(i_{upj} + i_{lowj}) - \frac{i_{dc}}{3},$$

$$\frac{V_{dc}}{2} - \frac{v_{lowj} + v_{upj}}{2} = l \frac{di_{zj}}{dt}.$$

# SM Capacitor Voltage Balancing

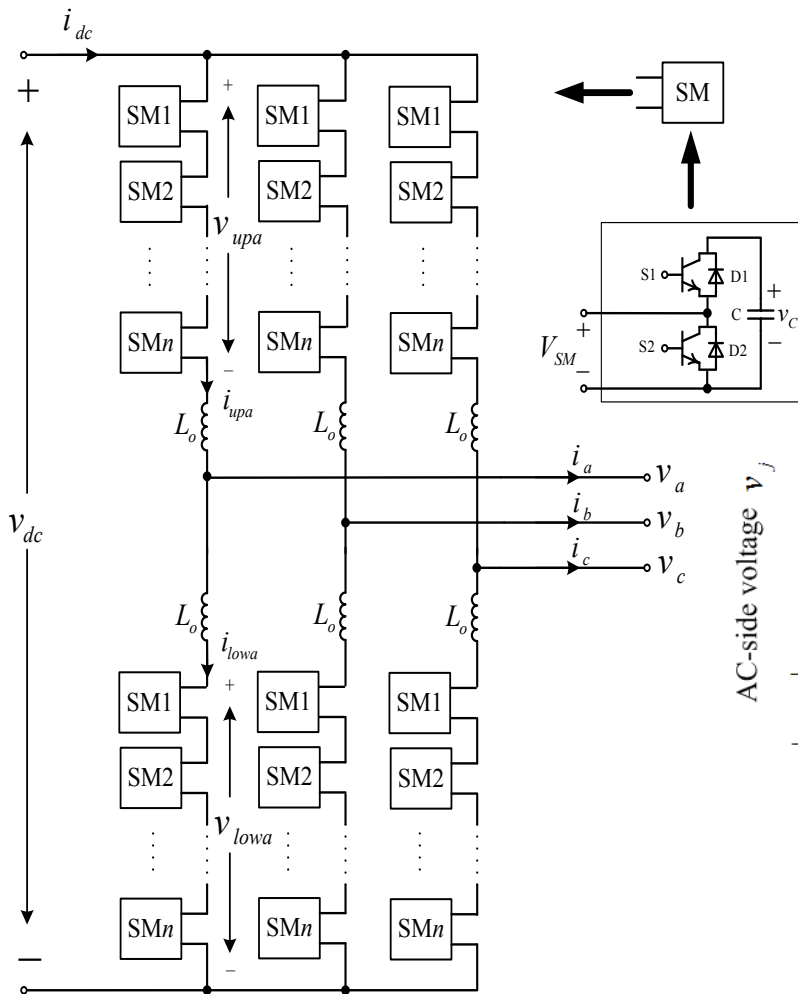

AC-side voltage  $v_j$

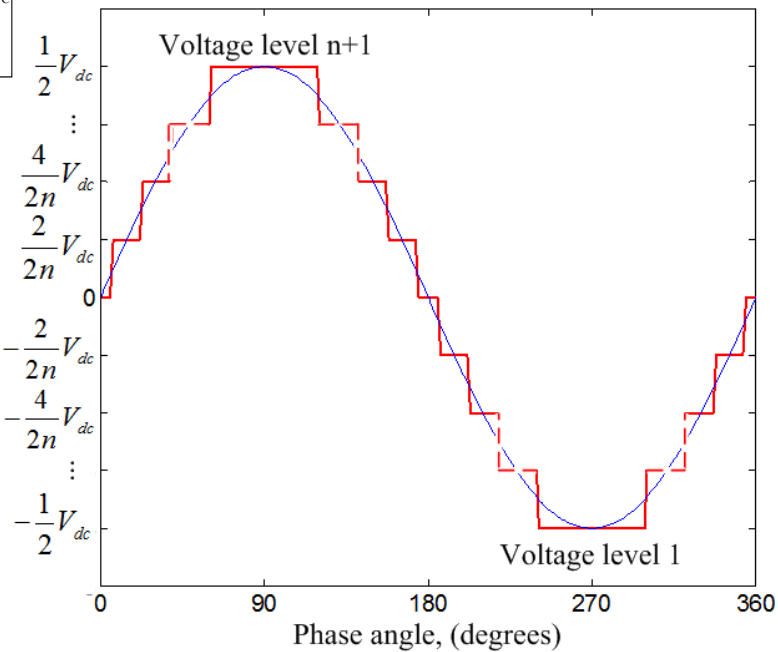

$$n_{p,j} = 0, \quad n_{n,j} = n$$

$$n_{p,j} = 1, \quad n_{n,j} = n - 1$$


$$\vdots$$

$$n_{p,j} = n - 1, \quad n_{n,j} = 1$$


$$n_{p,j} = n, \quad n_{n,j} = 0$$

# SM Capacitor Voltage Balancing

Example: Five-Level MMC

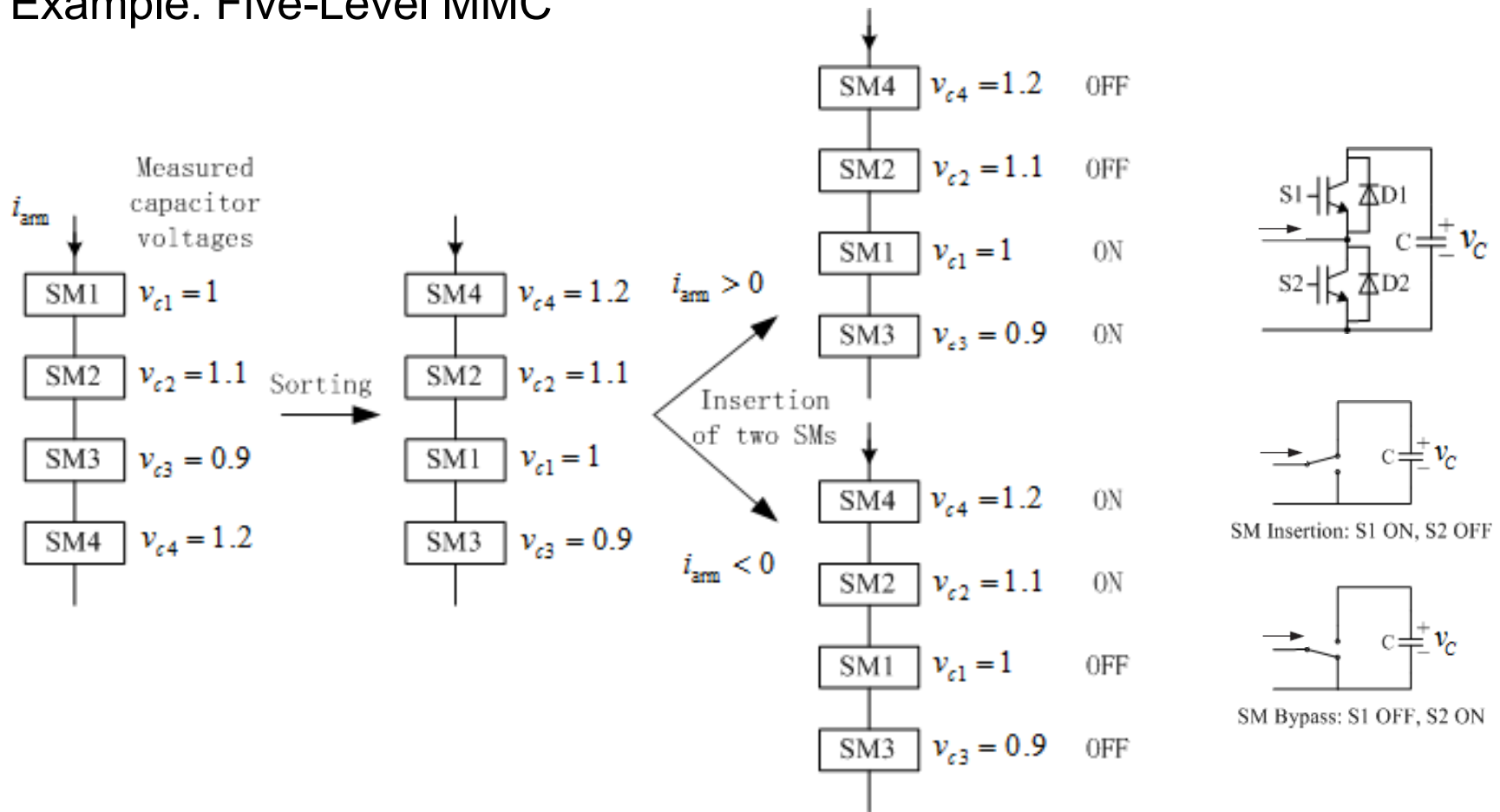

# Circulating Current Control

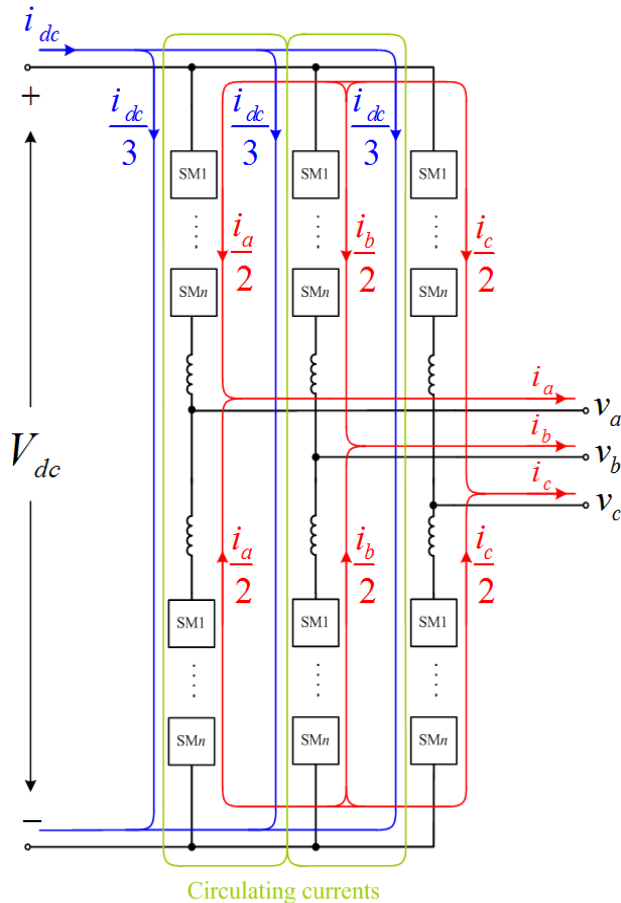

## High circulating current:

- Rating value/size of components
- SM capacitor voltage ripple
- Power losses

$$i_j = i_{upj} - i_{lowj}.$$

$$i_{zj} = \frac{1}{2}(i_{upj} + i_{lowj}) - \frac{i_{dc}}{3},$$

$$\frac{V_{dc}}{2} - \frac{v_{lowj} + v_{upj}}{2} = l \frac{di_{zj}}{dt}.$$



# Circulating Current Control

- Circulating current – contains 2<sup>nd</sup> harmonic predominantly
- Controllers to eliminate circulating current:
  - Proportional Resonant (PR) Controller
  - Predictive Circulating Current Controller

# Circulating Current Control: PR Controller

- Circulating current dynamics:


$$L_o \frac{di_{z,abc}}{dt} + R_o i_{z,abc} = v_{z,abc} \approx m_{z,abc} V_{dc}$$

- PR Controller:


$$K_{p1} + \frac{K_{i1}s}{s^2 + \omega_{n1}^2} + \frac{K_{i2}s}{s^2 + \omega_{n2}^2}$$

- $\omega_{n1}$  and  $\omega_{n2}$  are tuned to 2<sup>nd</sup> and 4<sup>th</sup> harmonic.
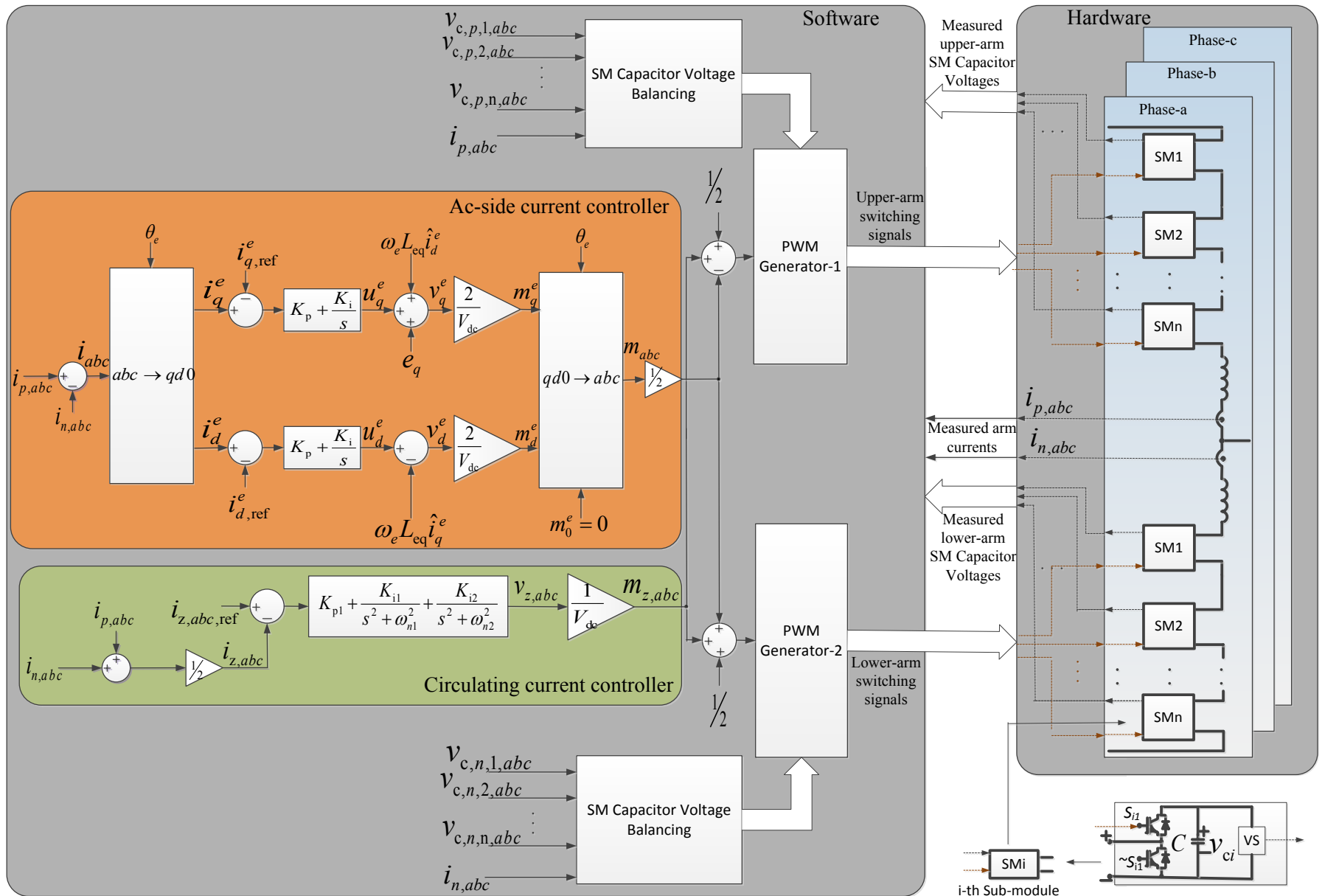
# Circulating Current Control: PR Controller


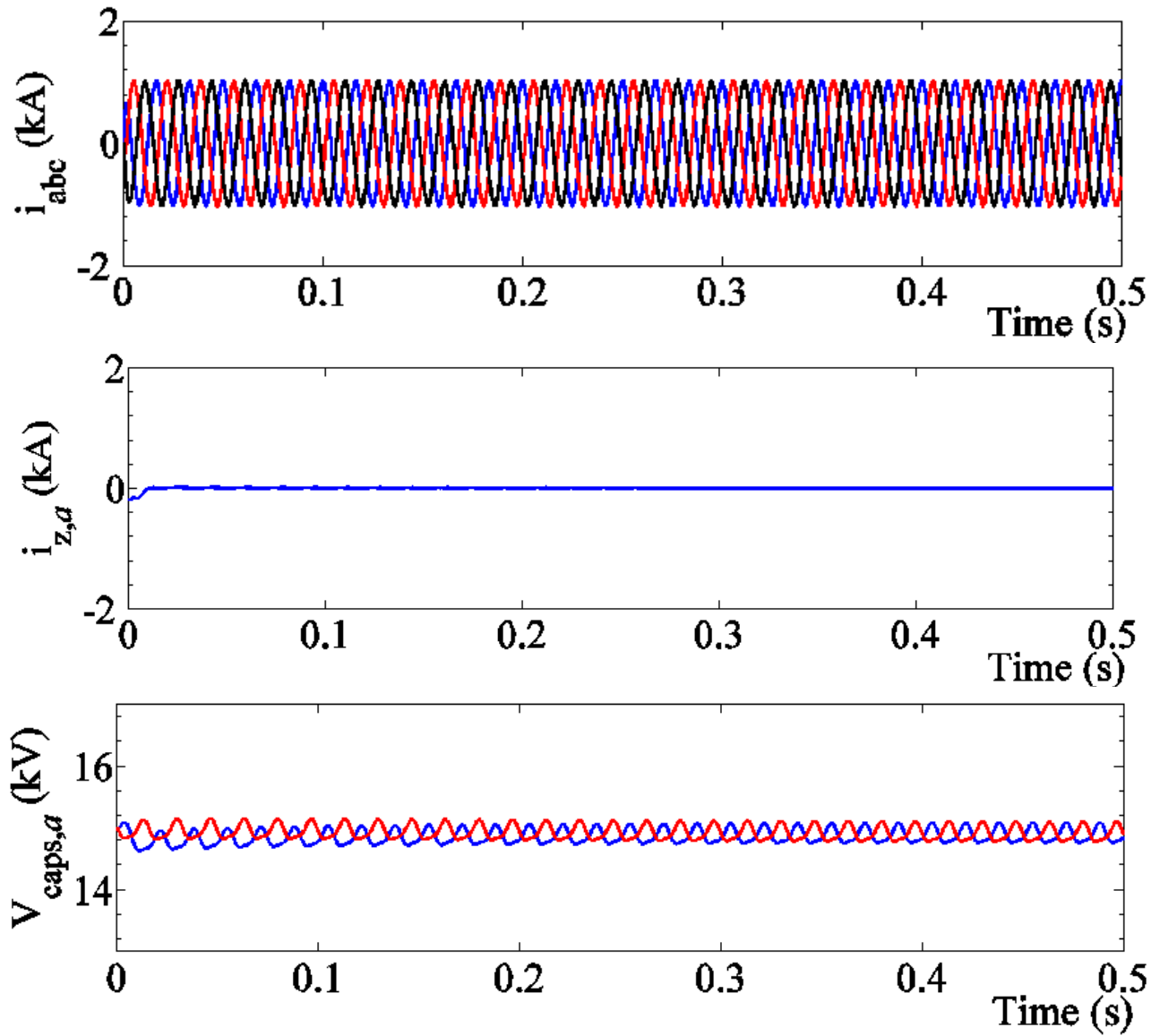
# Circulating Current Control: PR Controller



# Circulating Current Control: Predictive Current Controller

From KVL:


$$\frac{V_{dc}}{2} - v_{upa} = l \frac{di_{upa}}{dt} + Ri_a + L \frac{di_a}{dt} + v_{sa},$$

$$\frac{V_{dc}}{2} - v_{lowa} = l \frac{di_{lowa}}{dt} - Ri_a - L \frac{di_a}{dt} - v_{sa}$$

Discrete model of the ac-side phase current:

$$i_a(k+1) = \frac{1}{K'} \left( \frac{v_{lowa}(k+1) - v_{upa}(k+1)}{2} - v_{sa}(k+1) + \frac{L'}{T_s} i_a(k) \right) \frac{V_{dc}}{2}$$
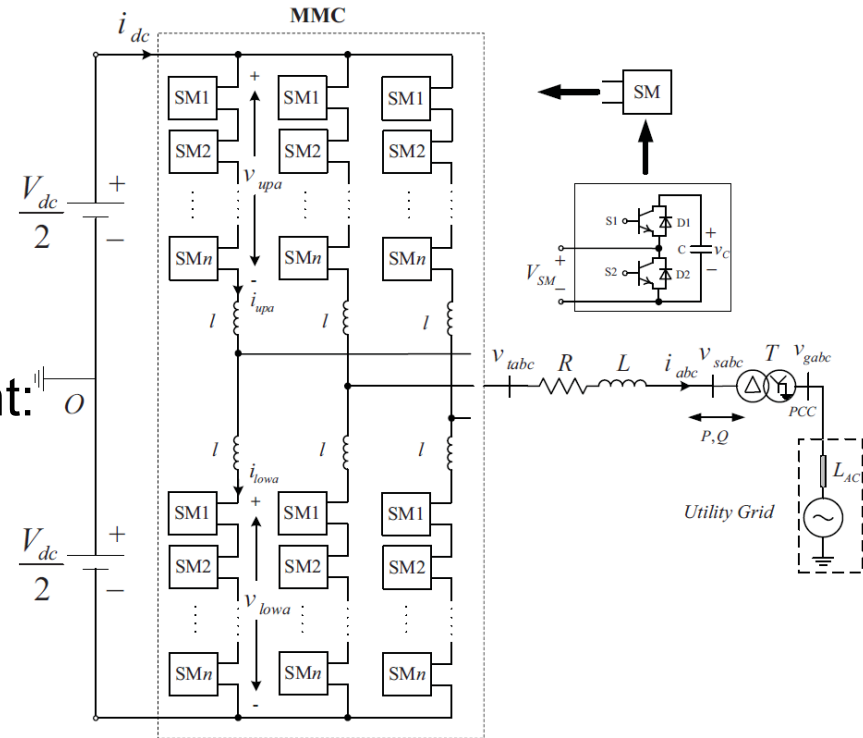
$$L' = \frac{l}{2} + L \quad K' = \frac{L'}{T_s} + R$$




Discrete model for circulating current and SM capacitor voltages:

$$i_z(k+1) = \frac{T_s}{2l} (V_{dc} - v_{lowa}(k+1) - v_{upa}(k+1)) + i_z(k)$$

$$V_{cij}(k+1) = V_{cij}(k) + \frac{i_l(k)}{C} T_s$$

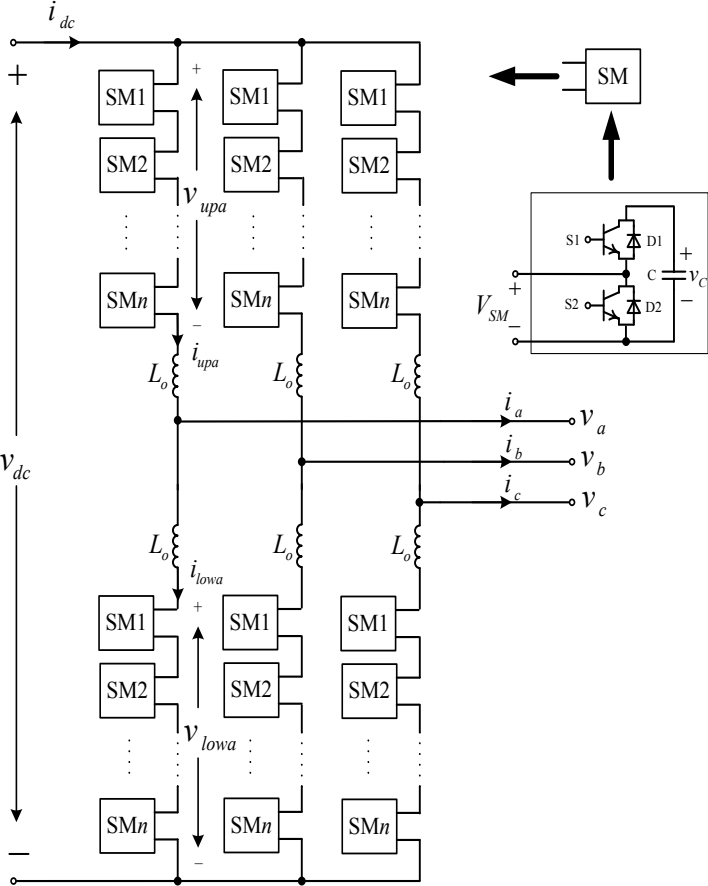
# Predictive Circulating Current Control of MMC

Prediction based on cost function minimization:













$$J = \lambda \left( \sum_i \left| V_{cij} - \frac{V_{dc}}{n} \right| \right) + \lambda_z |i_{zj}|$$

# Closed-Loop Control of MMC-HVDC

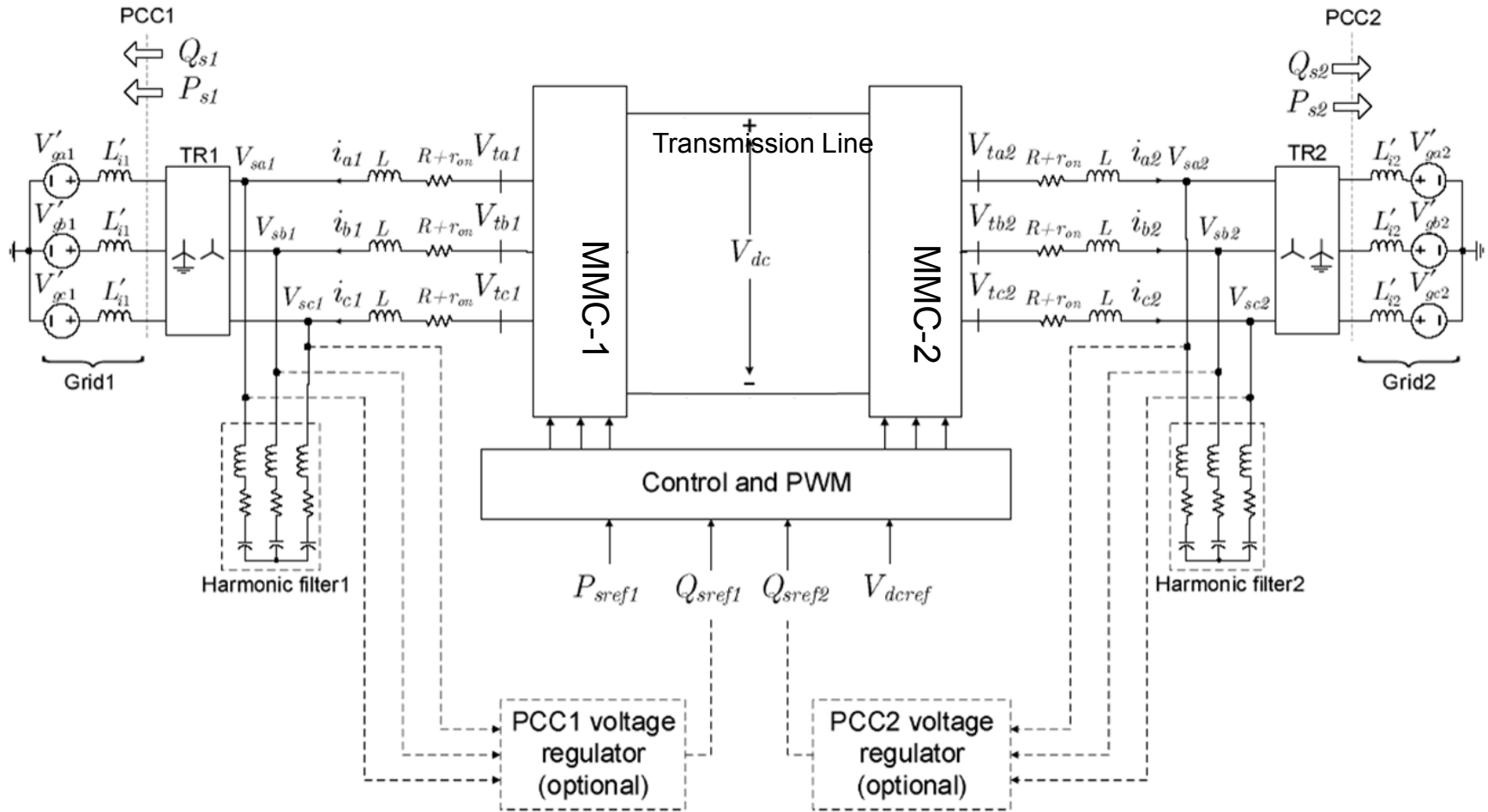



# Predictive Control of MMC-HVDC

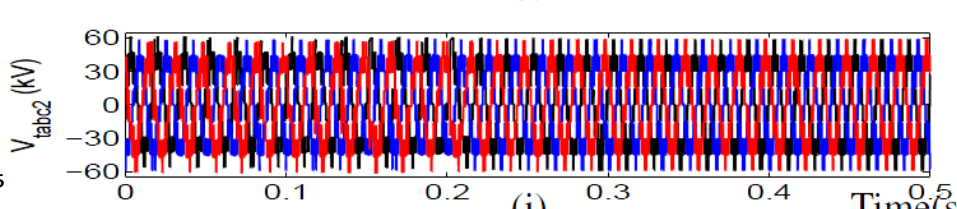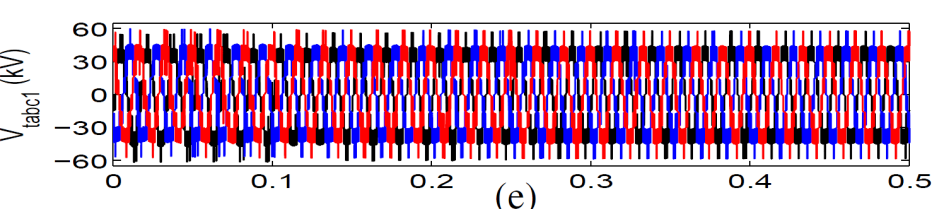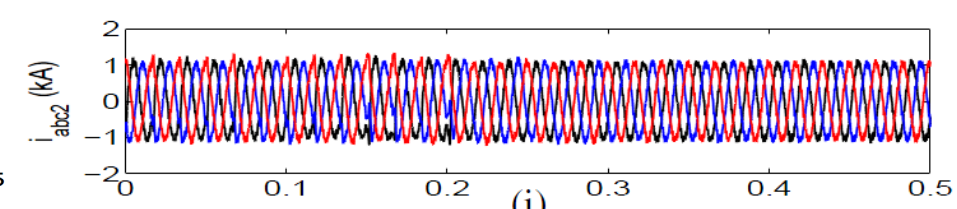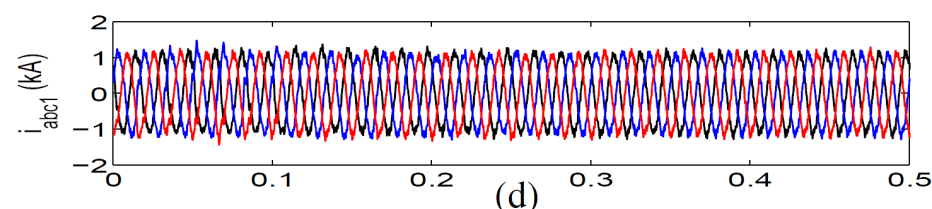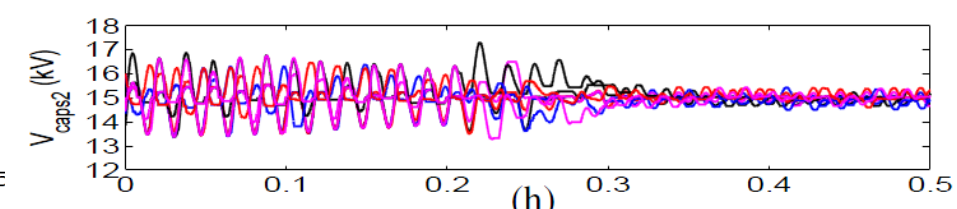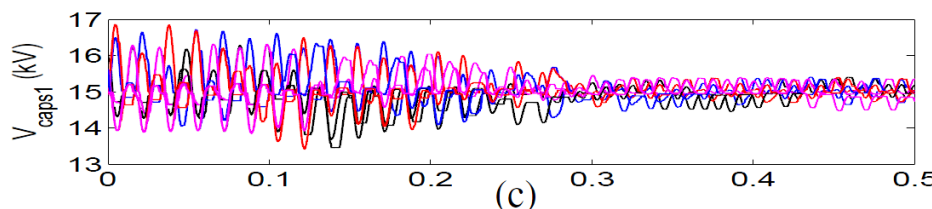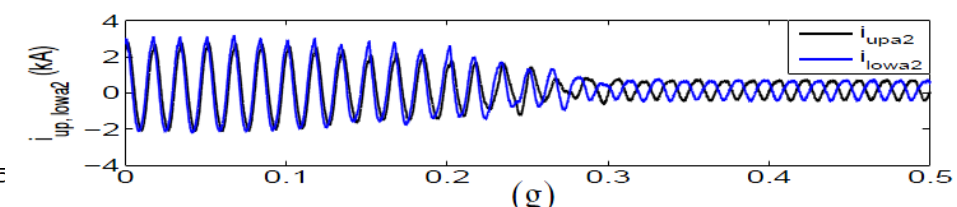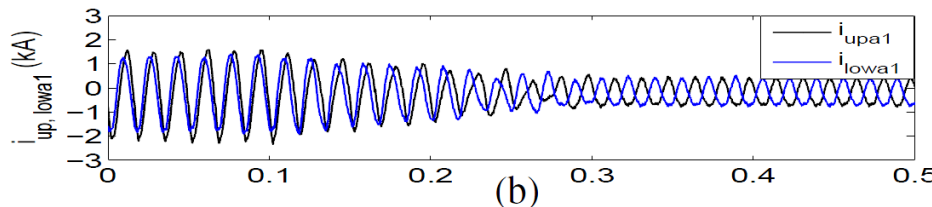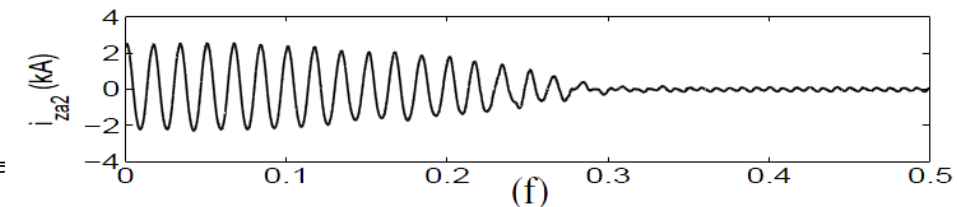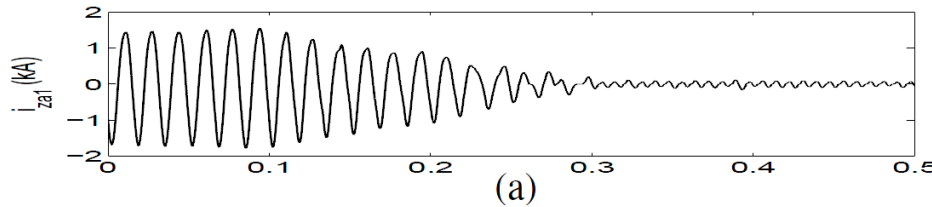

Time(s)





# DC-Side Fault in MMC-HVDC Systems

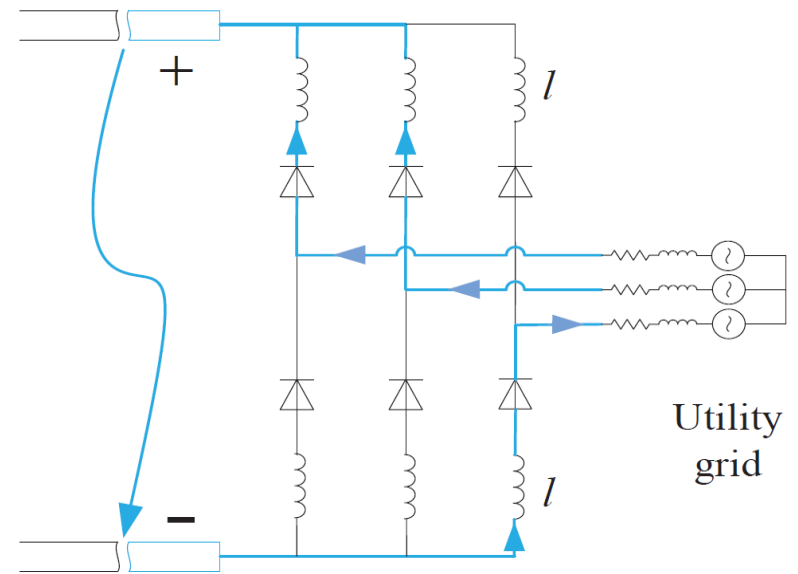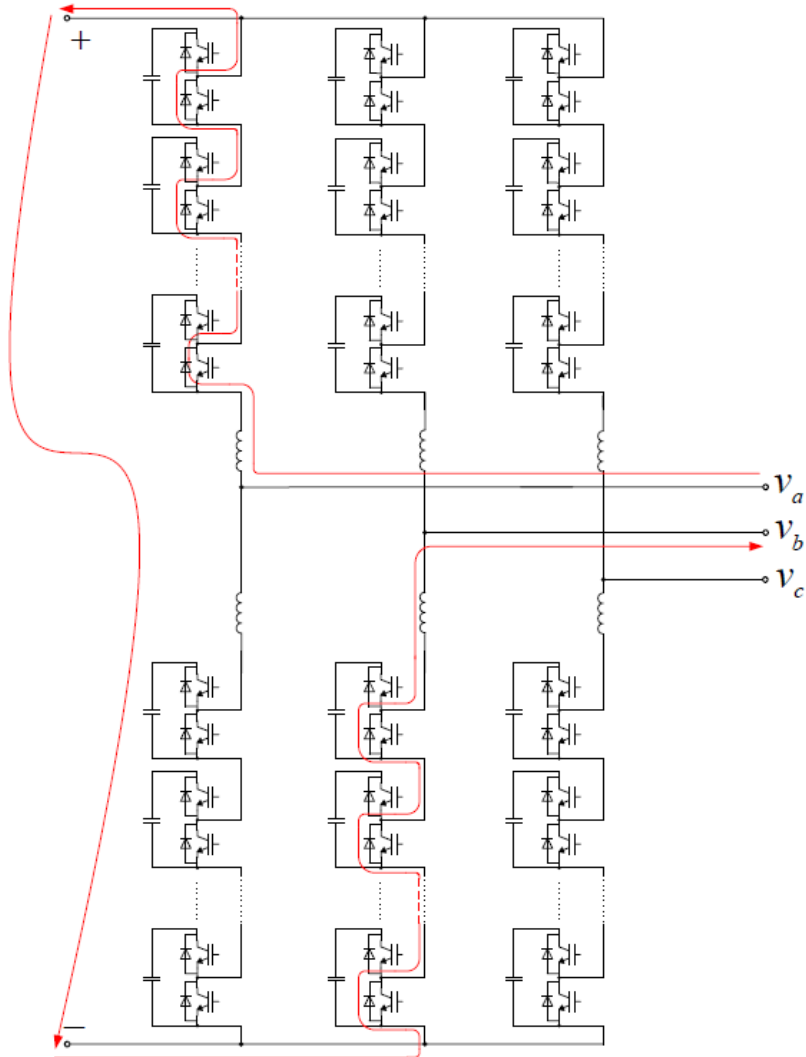


# SM Technologies: Normal Operation


## Full-Bridge SM

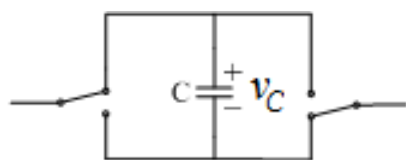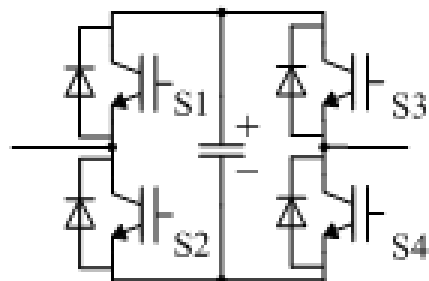

SM Insertion: S1, S4 ON; S2, S3 OFF


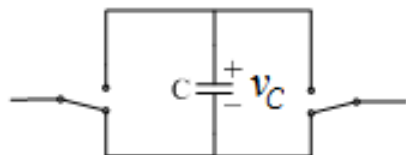


SM Bypass: S1, S3 OFF, S2, S4 ON

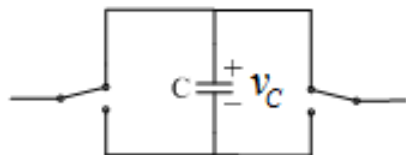


SM Bypass: S1, S3 ON, S2, S4 OFF


## Clamp-Double SM

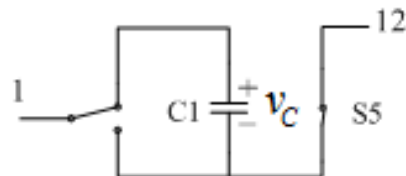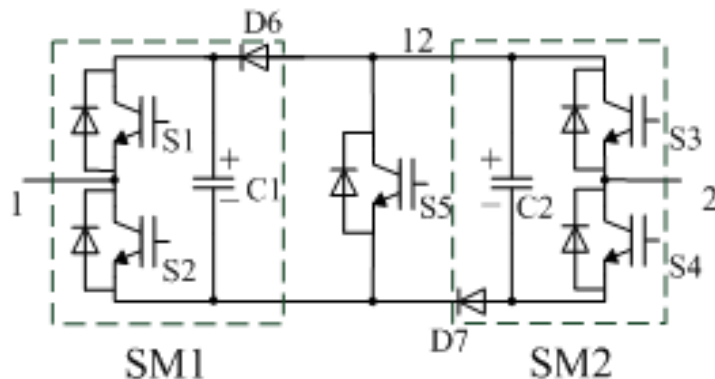


SM1 Insertion: S1 ON, S2 OFF

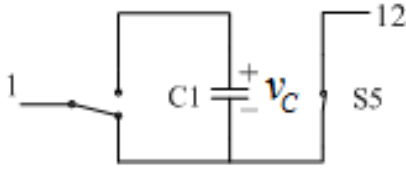

SM1 Bypass: S1 OFF, S2 ON

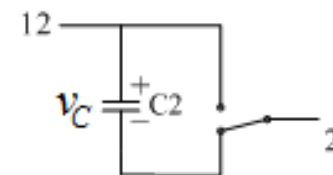


SM2 Insertion: S4 ON, S3 OFF

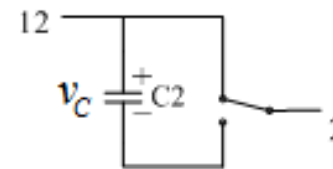


SM2 Bypass: S4 OFF, S3 ON

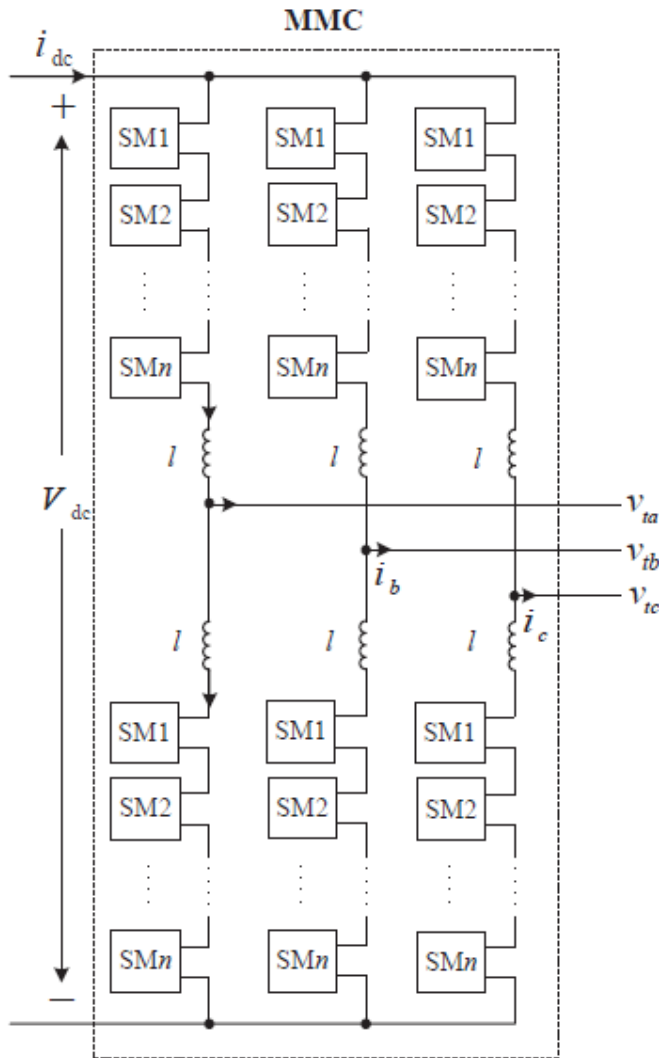
# SM Technologies: DC-side Short-Circuit Fault Operation




Full-Bridge SM

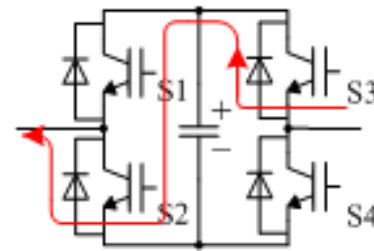








Clamp-Double SM

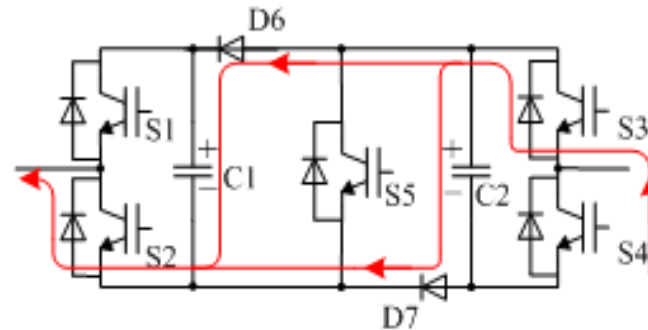
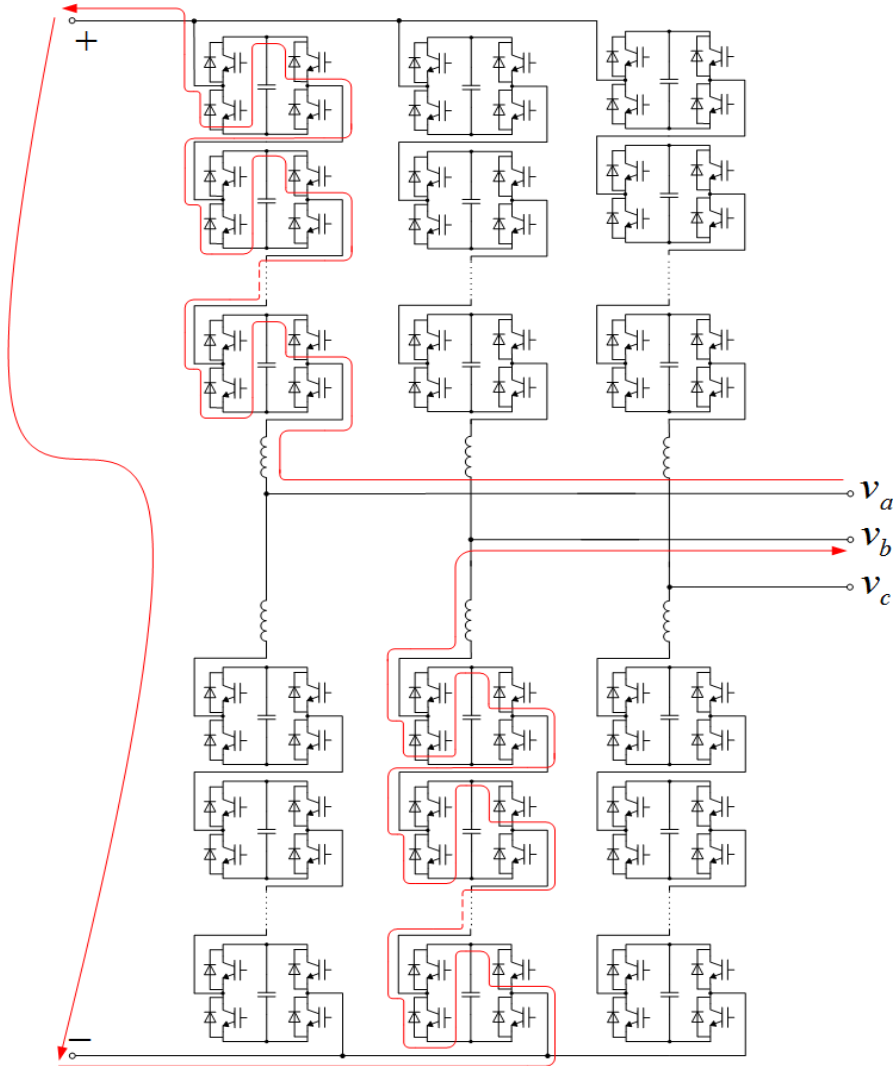
# DC-side Short-Circuit Fault Operation of Full-Bridge MMC



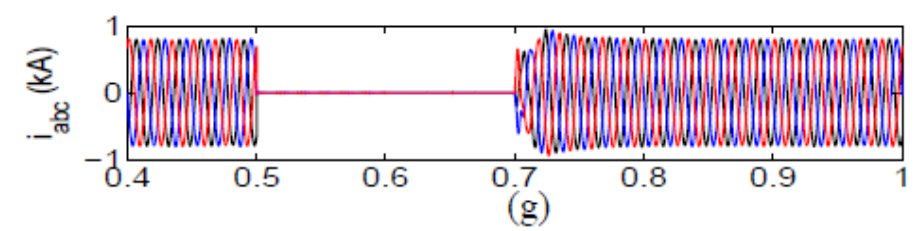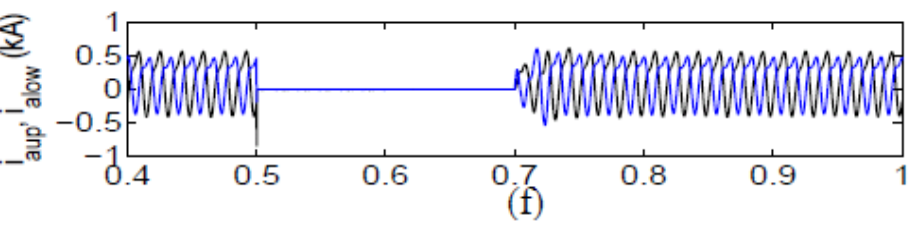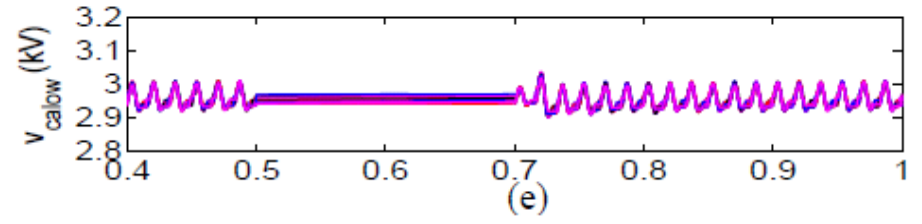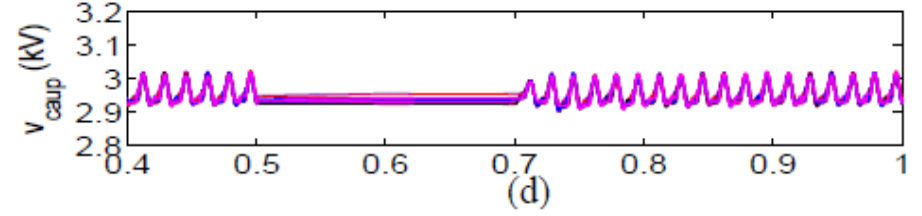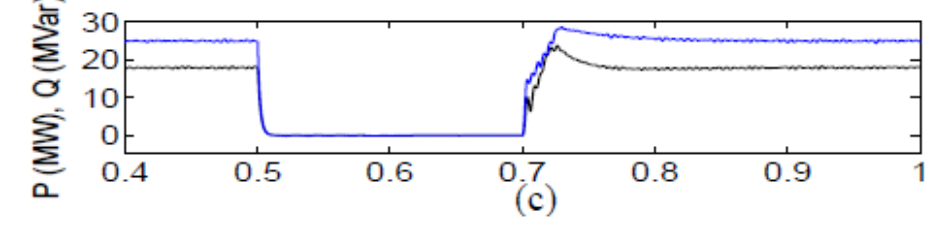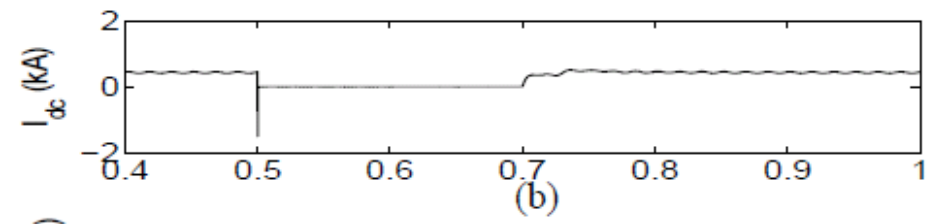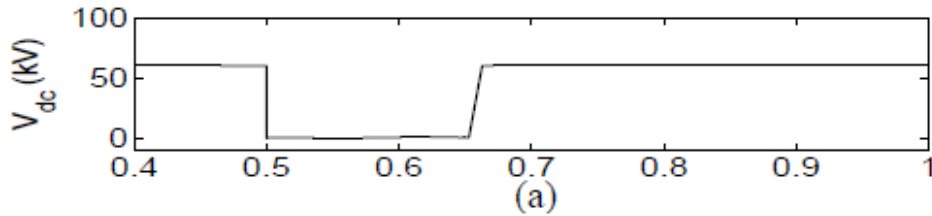
# DC-Side Fault in MMC-HVDC Systems: Full-Bridge MMC Case



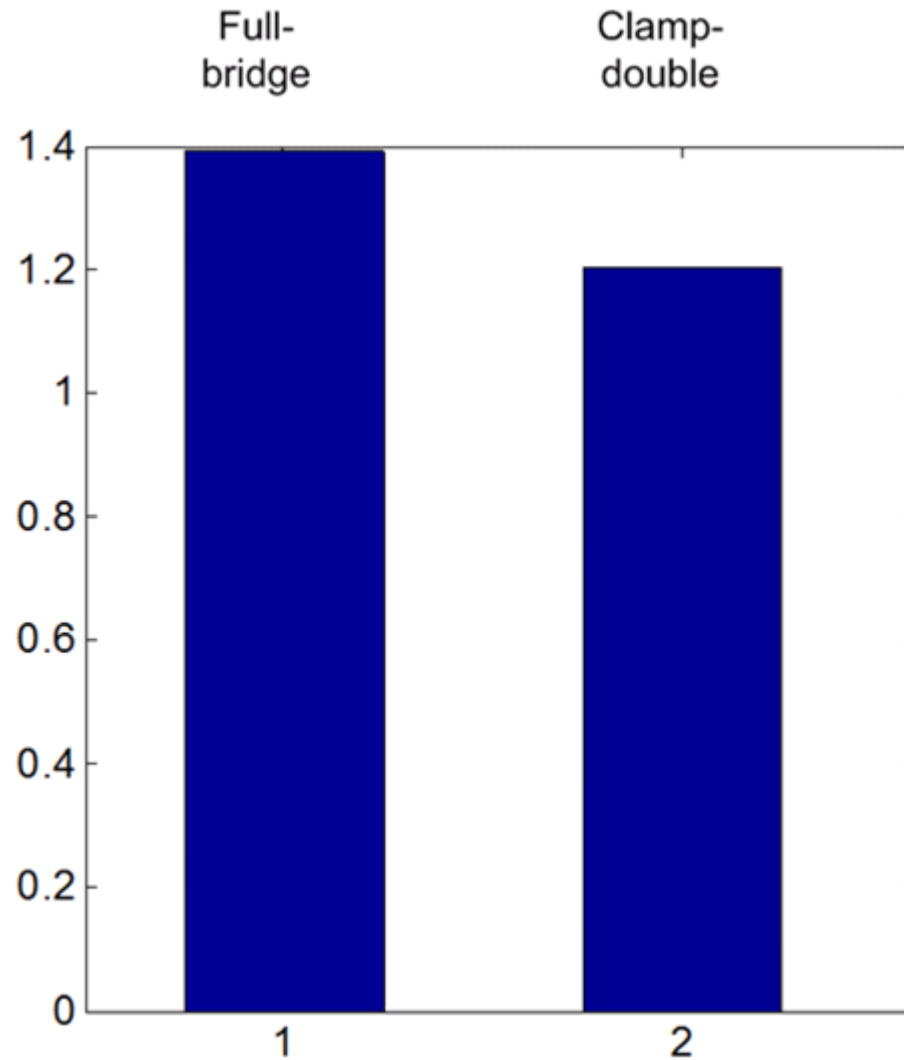
# Power Losses for Various SM Circuits

Power Losses of Single SM-type MMCs Normalized with Respect to Half-Bridge MMC










# Hybrid Design of MMC-HVDC Systems

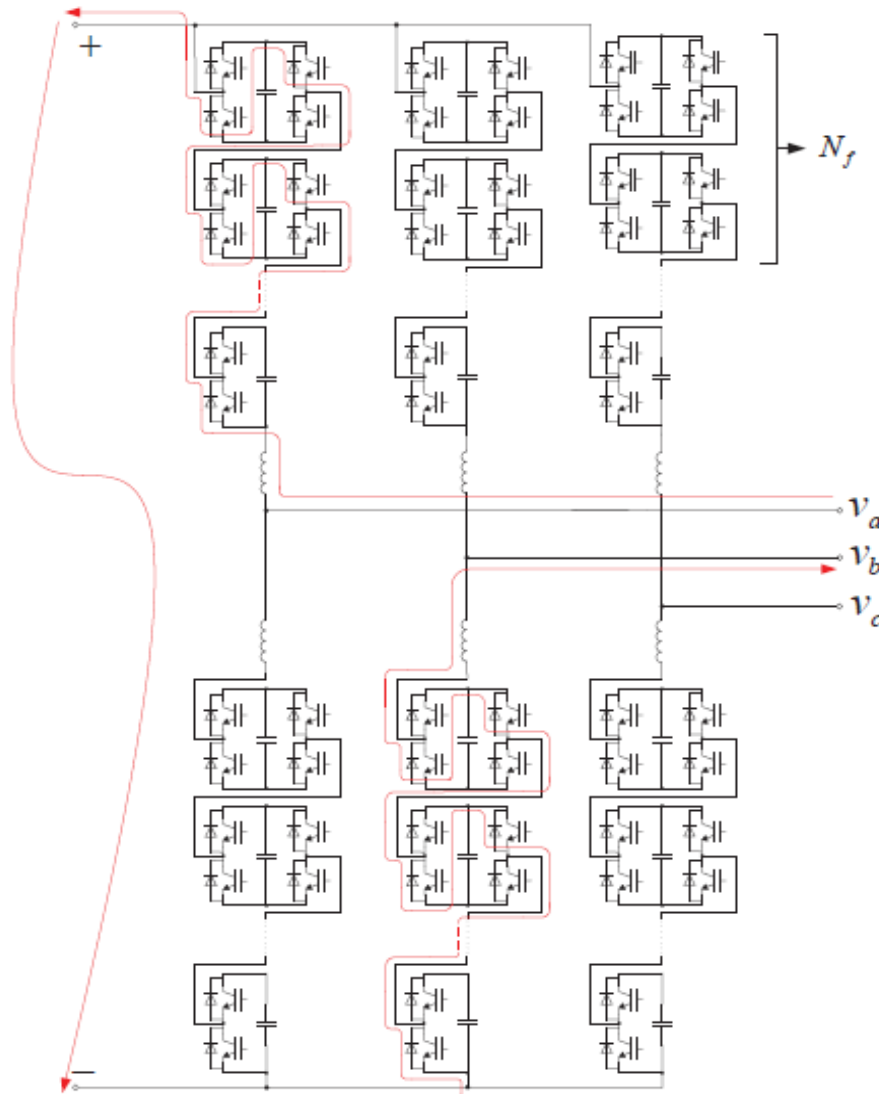

$$N_f \geq \frac{V_{\text{amp\_LL}}}{2V_{\text{cap\_ref}}}$$

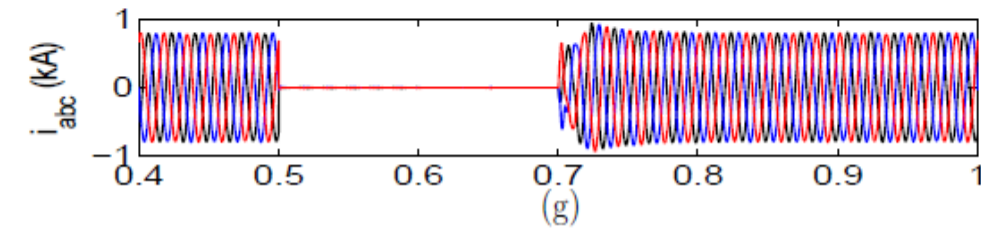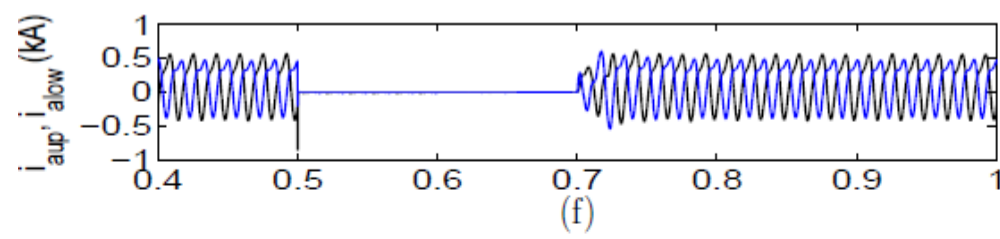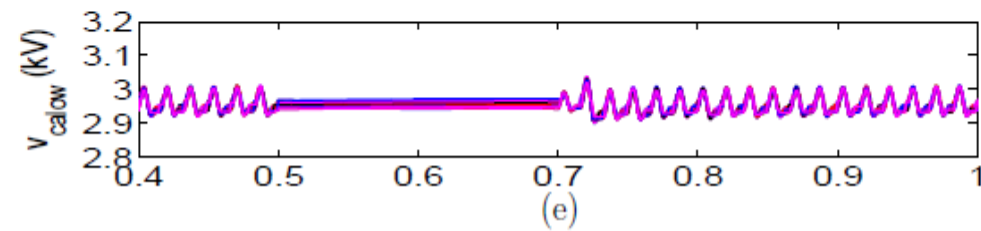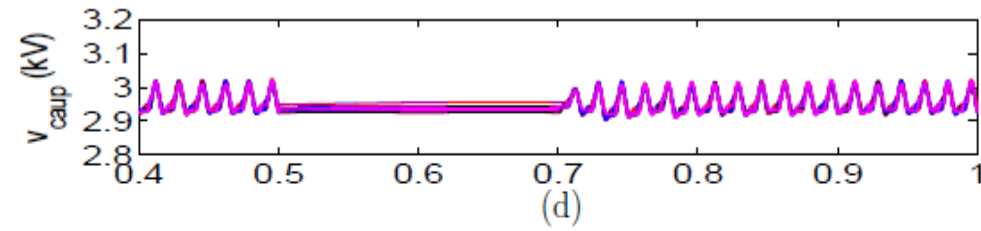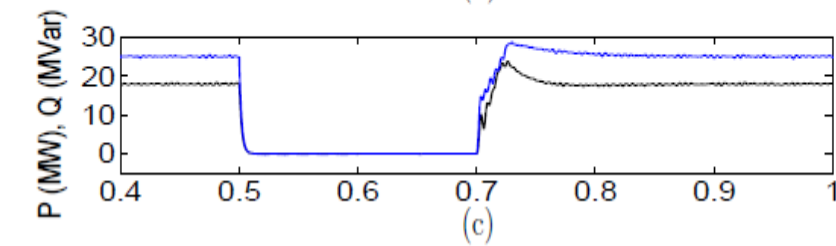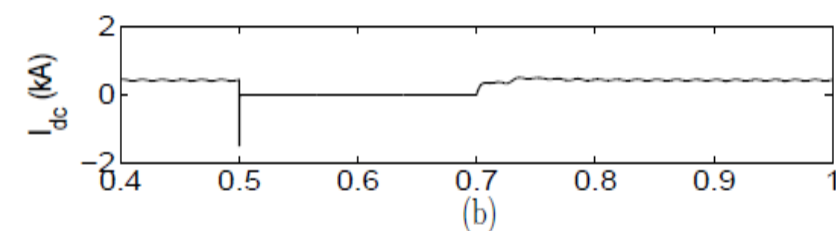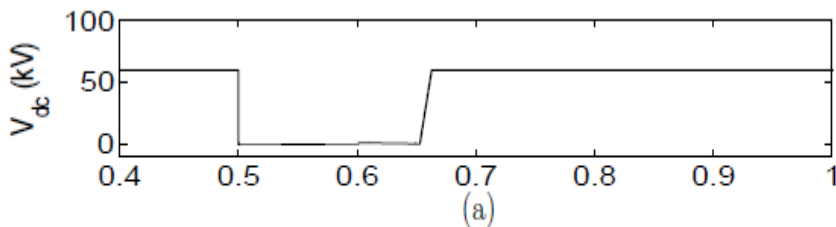
# DC-Side Fault in MMC-HVDC Systems: Hybrid MMC Case




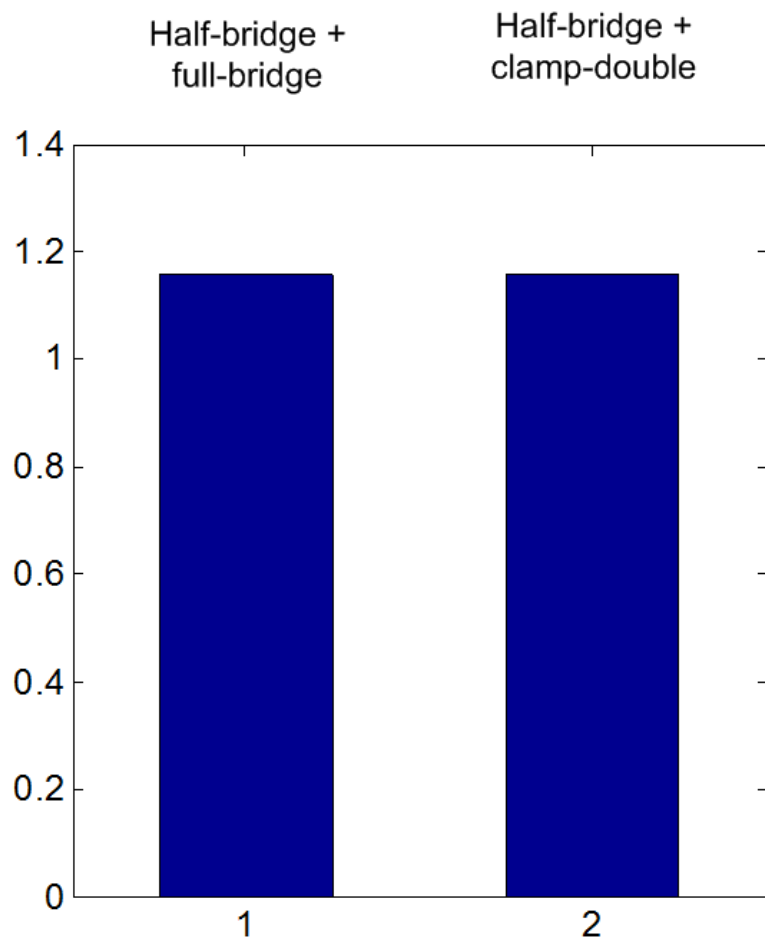
# Power Losses for Various Hybrid MMCs

Power Losses  
of Hybrid  
MMCs  
Normalized  
with Respect  
to Half-Bridge  
MMC



# Future Work

- Control and protection of multi-terminal HVDC systems based on the MMC
- Accurate and efficient modeling and simulation tools for MMC-HVDC systems
- Operation of the MMC-HVDC systems under fault conditions

# Acknowledgement

- This presentation contains data and graphs from ABB publications/presentations available on the public domain including:
- Mats Larsson, Corporate Research, ABB Switzerland Ltd, “HVDC and HVDC Light: An alternative power transmission system”, Symposium on Control & Modeling of Alternative Energy Systems, April 2, 2009.
- Gunnar Persson, Senior Project Manager, Power Systems - HVDC, ABB AB Sweden, “HVDC Converter Operations and Performance, Classic and VSC”, Dhaka, September 18, 2011.